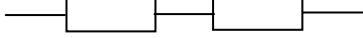


## Exercices dipôles résistifs


Dans chacun des cas ci-dessous, calculer la résistance équivalente du groupement:

$$R_1 = 100 \, \Omega \quad R_2 = 50 \, \Omega$$



$$R_{eq} = ?$$


$$R_1 = 100 \, \Omega$$

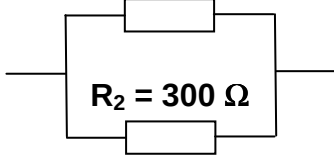

$$R_2 = 300 \, \Omega$$

$$R_{eq} = ?$$

$$R_1 = 60 \, \Omega$$

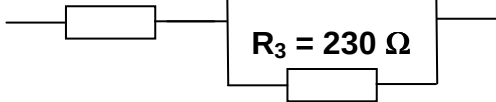


$$R_2 = 130 \, \Omega$$

$$R_3 = 230 \, \Omega$$

$$R_{eq} = ?$$

$$R_{eq} = ?$$

$$R_1 = 10 \, \Omega$$

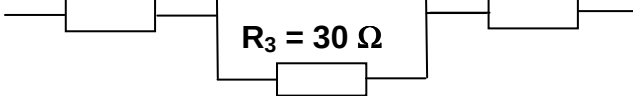


$$R_2 = 120 \, \Omega$$

$$R_3 = 30 \, \Omega$$

$$R_4 = 50 \, \Omega$$

$$R_{eq} = ?$$

$$R_1 = 100 \, \Omega$$

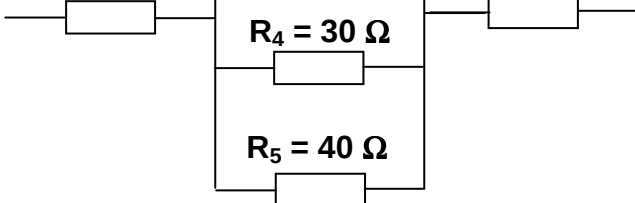

$$R_2 = 10 \, \Omega$$

$$R_3 = 20 \, \Omega$$

$$R_4 = 30 \, \Omega$$

$$R_5 = 40 \, \Omega$$

$$R_6 = 50 \, \Omega$$

