
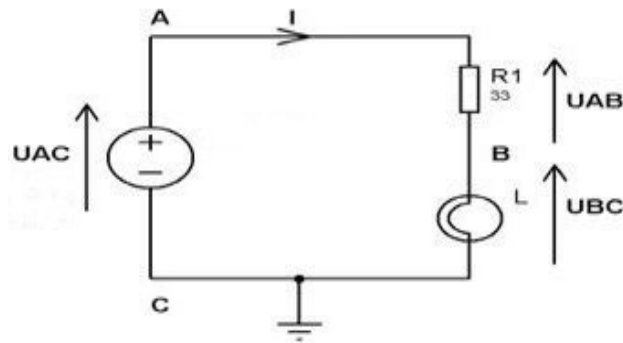


Exercice 1 Solution

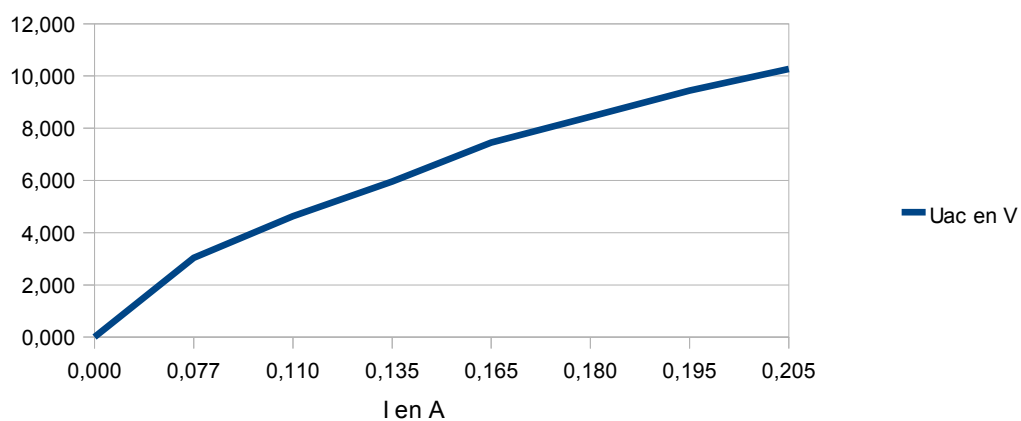

VILLERS

I en A	Ubc en V	Uab en volt	Uac en V
0,000	0,000	0,000	0,000
0,077	0,500	2,541	3,041
0,110	1,000	3,630	4,630
0,135	1,500	4,455	5,955
0,165	2,000	5,445	7,445
0,180	2,500	5,940	8,440
0,195	3,000	6,435	9,435
0,205	3,500	6,765	10,265



Lorsque $U_{ac} = 7,5V$, alors graphiquement I vaut $0,16 A$ environ

Exercise 1 Solution