

### Charge du condensateur

t (s)	0	$T$	$2.T$	$3T$	$4T$	$5T$
$U_c$ (V)	0 %					99 %

### Décharge du condensateur

t (s)	0	$\tau$	$2.\tau$	$3\tau$	$4\tau$	$5\tau$
$U_c$ (V)	$U_{c0}$					1 %

